

13. CURRENT ELECTRICITY

1. A cell of e.m.f. 3 V and internal resistance 4 Ω is connected to two resistances of 10 Ω and 24 Ω joined in parallel. Find the current through each resistance using Kirchhoff's laws.

Given :

$$\begin{aligned} E &= 3 \text{ V} \\ r &= 4 \Omega \\ R_1 &= 10 \Omega \\ R_2 &= 24 \Omega \end{aligned}$$

To Find :

$$\begin{aligned} I_1 &= \text{Current through } R_1 = ?, \\ I_2 &= \text{Current through } R_2 = ?, \\ I &= \text{Total current through network} \end{aligned}$$

Formula :


- i) $\Sigma I = 0$ (Kirchhoff's Junction law)
- ii) $\Sigma IR + \Sigma E = 0$ (Kirchhoff's voltage law)

Solution :

From Kirchhoff's junction law,

$$I - I_1 - I_2 = 0$$

$$\therefore I = I_1 + I_2$$

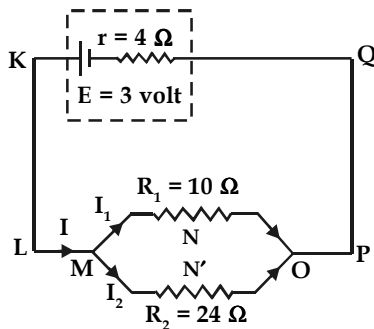

Apply Kirchhoff's voltage law for loop in the circuit containing KLMNOPQK

$$-I_1 R_1 - Ir + E = 0$$

$$\therefore -I_1 R_1 - (I_1 + I_2) r + E = 0$$

$$\therefore -10 I_1 - 4 (I_1 + I_2) + 3 = 0$$

$$\therefore -10 I_1 - 4 I_1 - 4 I_2 + 3 = 0$$

$$\therefore -14 I_1 - 4 I_2 + 3 = 0$$

Current Electricity

$$\therefore 14 I_1 + 4 I_2 = 3 \quad \dots (i)$$

Apply Kirchhoff's voltage law for loop MN'ONM

$$-I_2 R_2 + I_1 R_1 = 0$$

$$-24 I_2 + 10 I_1 = 0$$

$$\therefore I_1 = 2.4 I_2 \quad \dots (ii)$$

From equations (i) and (ii)

$$14 (2.4 I_2) + 4 I_2 = 3$$

$$\therefore 33.6 I_2 + 4 I_2 = 3$$

$$\therefore 37.6 I_2 = 3$$

$$\therefore I_2 = \frac{3}{37.6}$$

$$I_2 = 0.07979 \text{ A} \quad \dots (iii)$$

From equations (ii) and (iii)

$$I_1 = 2.4 \times 0.07979$$

$$= 0.1914 \text{ A} \quad \dots (iv)$$

$$\begin{aligned} I &= I_1 + I_2 \\ &= 0.1914 + 0.07979 \\ &= 0.27119 \end{aligned}$$

$$\therefore I_1 = 0.194 \text{ A}$$

$$I_2 = 0.0798 \text{ A}$$

$$I = 0.2712 \text{ A}$$

2. The current flowing through an external resistance of 2 Ω is 0.5 A, when it is connected to the terminals of a cell. This current reduces to 0.25 A when the external resistance is 5 Ω . Use Kirchhoff's laws to find e.m.f of cell.

Given :

$$R_1 = 2 \Omega$$

$$R_2 = 5 \Omega$$

$$I_1 = 0.5 \text{ A},$$

$$I_2 = 0.25 \text{ A}$$



To Find :

$$E = ?$$

Formula :

$$\Sigma IR + \Sigma E = 0$$

Solution :

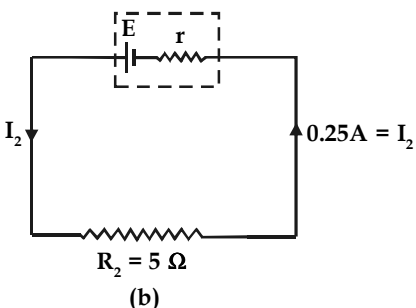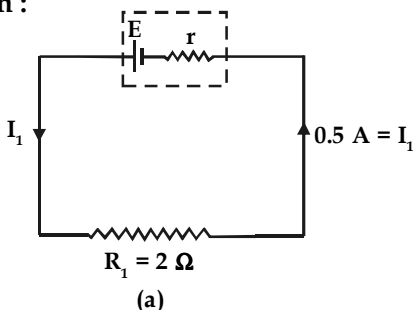

Let r be the internal resistance of cell E .
Apply Kirchoff's voltage law to figure (a)

$$- I_1 (R_1 + r) + E = 0$$

$$\therefore E = I_1 (R_1 + r) \quad \dots (i)$$

$$E = 0.5 (2 + r)$$

Apply Kirchoff's voltage law to figure (b)

$$- I_2 (R_2 + r) + E = 0$$

$$\therefore E = I_2 (R_2 + r) \quad \dots (ii)$$

$$E = 0.25 (5 + r)$$

From equations (i) and (ii)

$$0.5 (2 + r) = 0.25 (5 + r)$$

$$\therefore 2 (2 + r) = (5 + r)$$

$$\therefore 4 + 2r = 5 + r$$


$$\therefore r = 1 \Omega \quad \dots (iii)$$

From equations (i) and (iii)

$$E = 0.5 (2 + 1) = 1.5 \text{ volt}$$

$$\therefore E = 1.5 \text{ V}$$

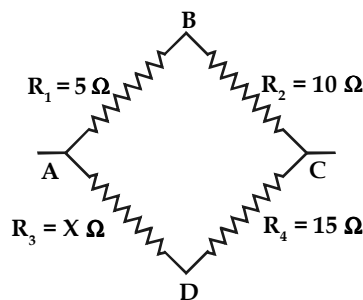3. Four resistances 5Ω , 10Ω , 15Ω and an unknown $X \Omega$, are connected in series so as to form Wheatstone's network. Determine the unknown resistance X , if the network is balanced with these numerical values of resistances.



Given :

$$R_1 = 5 \Omega$$

$$R_2 = 10 \Omega$$

$$R_4 = 15 \Omega$$

To Find :

$$X = ?$$

Formula :

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Solution :

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\therefore R_3 = \frac{R_1}{R_2} \times R_4$$

$$\therefore R_3 = \frac{5}{10} \times 15 = 7.5$$

$$\therefore X = 7.5 \Omega$$

4. In a meter-bridge experiment with resistance R_1 in left and resistance X in right gap, null point is obtained at 40 cm from left end. With a resistance R_2 in left gap and same resistance X in right gap, null point is obtained at 50 cm from left end. Where will be null point if R_1 and R_2 are put first in series and then in parallel, in the left gap and right gap still containing X ?

Solution :

When R_1 is in left gap and X is in right gap,

$$\text{null point} = l_{R_1} = 40 \text{ cm}$$

When R_2 is in left gap and X in right gap,

$$\text{null point} = l_{R_2} = 50 \text{ cm}$$

For R_1 and R_2 in series with left gap, null point $l_s = ?$

For R_1 and R_2 in parallel in left gap, null point $l_p = ?$

In balanced position

$$\frac{R_1}{X} = \frac{l_R}{l_x}$$

For first case, $l_{R_1} = 40 \text{ cm}$

$$\therefore l_{x_1} = 100 - 40 = 60 \text{ cm}$$

$$\therefore l_{x_1} = 60 \text{ cm}$$

$$\therefore \frac{R_1}{X} = \frac{l_{R_1}}{l_{x_1}}$$

$$\therefore R_1 = \frac{l_{R_1}}{l_{x_1}} \times X = \frac{40}{60} \times X$$

$$\therefore R_1 = \frac{2X}{3} \quad \dots(i)$$

For second case, $l_{R_2} = 50 \text{ cm}$

$$\therefore l_{x_2} = 100 - 50$$

$$l_{x_2} = 50 \text{ cm}$$

$$\therefore \frac{R_2}{X} = \frac{l_{R_2}}{l_{x_2}}$$

$$\therefore R_2 = \frac{l_{R_2}}{l_{x_2}} X = \frac{50}{50} X$$

$$\therefore R_2 = X \quad \dots(ii)$$

When R_1 and R_2 are connected in series, the equivalent resistance is given by

$$R_s = R_1 + R_2 = \frac{2X}{3} + X$$

$$\therefore R_s = \frac{5X}{3} \quad \dots(iii)$$

The null point in series combination is obtained at l_s from left end (X in right gap and series combination in left gap)

$$\therefore l_x = 100 - l_s$$

$$\frac{R_s}{X} = \frac{l_s}{l_x}$$

$$\therefore \frac{5X}{3} = \frac{l_s}{100 - l_s} \quad [\text{From (iii)}]$$

$$\therefore \frac{5}{3} = \frac{l_s}{100 - l_s}$$

$$\therefore 5(100 - l_s) = 3 l_s$$

$$\therefore 500 - 5l_s = 3 l_s$$

$$\therefore 500 = 8 l_s$$

$$\therefore l_s = \frac{500}{8}$$

$$\therefore l_s = 62.5 \text{ cm}$$

When R_1 and R_2 are connected in parallel the equivalent resistance is given by

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{\frac{2X}{3} \cdot X}{\frac{2X}{3} + X} = \frac{2X}{5}$$

$$\therefore R_p = \frac{2X}{5} \quad \dots(iv)$$

The null point in parallel combination is obtained at l_p from the left end (X in right gap and parallel combination in left gap)

$$\therefore l_x = 100 - l_p$$

$$\therefore \frac{R_p}{X} = \frac{l_p}{l_x}$$

$$\therefore \frac{2X}{5} = \frac{l_p}{100 - l_p}$$

$$\begin{aligned} \therefore \frac{2}{5} &= \frac{l_p}{100 - l_p} \\ \therefore 2(100 - l_p) &= 5 l_p \\ \therefore \frac{200 - 2l_p}{7l_p} &= \frac{5l_p}{200} \\ \therefore l_p &= \frac{200}{7} \\ \therefore l_p &= 28.6 \text{ cm} \end{aligned}$$

5. A potentiometer wire has a length of 2 m and resistance of 10 Ω. It is connected in series with resistance 990 Ω and a cell of e.m.f 2 V. Calculate the potential along the wire.

Given :

$$\begin{aligned} L &= 2 \text{ m} \\ R &= 10 \ \Omega \\ R_E &= 990 \ \Omega \\ E &= 2 \text{ V} \end{aligned}$$

To Find :

$$K = ?$$

Formula :

$$K = \frac{V}{L}$$

Solution :

Since

$$I = \frac{E}{R + R_E}$$

Also

$$V = IR = \left(\frac{E}{R + R_E} \right) \cdot R$$

$$= \left(\frac{2}{10 + 990} \right) \cdot 10$$

$$= \frac{20}{1000}$$

$$V = 2 \times 10^{-2} \text{ volt}$$

$$K = \frac{V}{L}$$

$$K = \frac{2 \times 10^{-2}}{2}$$

$$\therefore K = 10^{-2} \text{ V/m}$$

6. Two cells having unknown e.m.f E_1 and E_2 ($E_1 > E_2$) are connected in potentiometer circuit so as to assist each other. The null point is obtained at 8.125 m from the higher potential end. When cell E_2 is connected so as to oppose cell E_1 , the null point is obtained at 1.25 m from same end. Compare the e.m.f's of two cells.

Given :

$$\begin{aligned} l_1 &= 8.125 \text{ m} \\ l_2 &= 1.25 \text{ m} \end{aligned}$$

To Find :

$$\frac{E_1}{E_2} = ?$$

Formula :

$$\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2}$$

Solution :

$$\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2}$$

$$\frac{E_1}{E_2} = \frac{8.125 + 1.25}{8.125 - 1.25}$$

$$= \frac{9.375}{6.875}$$

$$\therefore \frac{E_1}{E_2} = 1.363$$

7. A potentiometer wire has a length 10 m and a resistance 20 Ω. Its terminals are connected to a battery of e.m.f 4 V and internal resistance 5 Ω. What are the distances at which null points are obtained when two cells of e.m.f 1.5 V and 1.3 V are connected so as to (i) assist and (ii) oppose each other ?

Given :

$$L = 10 \text{ m}$$

$$R = 20 \ \Omega$$

$$E = 4 \text{ V}$$

Internal resistance of cell,

$$r = 5 \ \Omega$$

$$E_1 = 1.5 \text{ V} \quad \text{and}$$

$$E_2 = 1.3 \text{ V}$$

To Find :

- i) l_1 = Null point when E_1 and E_2 are connected in assist = ?
- ii) l_2 = Null point when E_1 and E_2 are connected in oppose = ?

Formula :

$$\text{i) } E_1 + E_2 = Kl_1$$

$$\text{ii) } E_1 - E_2 = Kl_2$$

Solution :

i) Since,

$$K = \frac{V}{L} = \frac{IR}{L}$$

$$= \frac{E}{(R+r)} \cdot \frac{R}{L}$$

$$K = \frac{ER}{(R+r)L}$$

$$\therefore K = \frac{4 \times 20}{(20+5) \times 10} = \frac{4 \times 20}{25 \times 10}$$

$$K = 0.32 \text{ V/m}$$

When E_1 and E_2 are connected so as to assist then we have

$$\text{i) } E_1 + E_2 = Kl_1$$

$$\therefore l_1 = \frac{E_1 + E_2}{K} = \frac{1.5 + 1.3}{0.32}$$

$$\therefore l_1 = \frac{280}{32}$$

$$\therefore l_1 = 8.75 \text{ m}$$

$$\text{ii) } E_1 - E_2 = Kl_2$$

$$\therefore l_2 = \frac{E_1 - E_2}{K}$$

$$= \frac{1.5 - 1.3}{0.32}$$

$$= \frac{0.2}{0.32}$$

$$\therefore l_2 = 0.625 \text{ m}$$

8. A potentiometer wire of length 4 m and resistance 8Ω is connected in series with a battery of e.m.f 2 V and negligible internal resistance. If the e.m.f of cell balances against length of 217 cm of the wire, find the e.m.f. of cell. When a cell is shunted by a resistance of 15Ω , the balancing length is reduced by 17 cm. Find the internal resistance of cell.

Given :

$$L = 4 \text{ m}$$

$$R = 8 \Omega$$

$$E = 2 \text{ V}$$

$$r \approx 0$$

$$l_1 = 217 \text{ cm} = 2.17 \text{ m}$$

$$R = 15 \Omega$$

$$l_2 = (217 - 17)$$

$$= 200 \text{ cm} = 2 \text{ m}$$

To Find :

$$E_1 = ?$$

$$r = ?$$

Formula :

$$\text{i) } E = KL$$

$$\text{ii) } r = R \left[\frac{l_1}{l_2} - 1 \right]$$

Solution :

Since,

$$K = \frac{V}{L} = \frac{IR}{L}$$

$$= \frac{E}{(R+r)} \cdot \frac{R}{L}$$

$$K = \frac{ER}{(R+r)L}$$

$$K = \frac{2 \times 8}{(8+0) \times 4} = \frac{2 \times 8}{8 \times 4}$$

$$\therefore K = 0.5 \text{ V/m}$$

$$\begin{aligned}
 \text{i) } E &= Kl \\
 E_1 &= Kl_1 \\
 &= 0.5 \times 2.17 = 1.085 \\
 \therefore E_1 &= 1.085 \text{ V} \\
 \text{ii) } r &= R \left[\frac{l_1}{l_2} - 1 \right] \\
 r &= 15 \left[\frac{2.17}{2} - 1 \right] \\
 &= 15 [1.085 - 1] \\
 &= 15 \times 0.085 \\
 \therefore r &= 1.275 \Omega
 \end{aligned}$$

9. A voltmeter has a resistance of 100 Ω. What will be its reading when it is connected across a cell of e.m.f 2 V and internal resistance 20 Ω ?

Given :

$$\begin{aligned}
 R &= 100 \Omega \\
 r &= 20 \Omega \\
 E &= 2 \text{ V}
 \end{aligned}$$


To Find :

$$V = ?$$

Formula :

$$V = E - Ir$$

Solution :

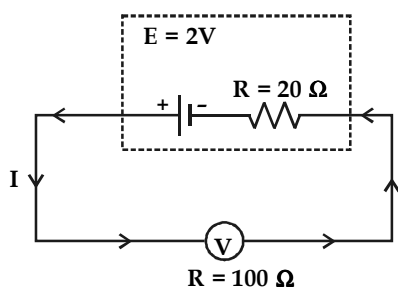

Current through the circuit is given by

$$\begin{aligned}
 I &= \frac{E}{R + r} \\
 &= \frac{2}{100 + 20}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{2}{120} \\
 \therefore I &= \frac{1}{60} \text{ A} \\
 V &= E - Ir \\
 V &= 2 - \left(\frac{1}{60} \times 20 \right) \\
 &= 2 - 0.3333 \\
 \therefore V &= 1.667 \text{ V}
 \end{aligned}$$

10. Four resistances 4 Ω, 4 Ω, 4 Ω and 12 Ω form a Wheatstone's network. Find the resistance which when connected across the 12 Ω resistance, will balance the network.

Given :

$$R_1 = R_2 = R_3 = 4 \Omega$$

To Find :

Resistance connected across 12 Ω resistance to balance the network = ?

Formula :

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Solution :

Let resistances connected across 12 Ω be X.

Equivalent resistance for 12 Ω and X in parallel is given by

$$X_p = \frac{12 \times X}{12 + X}$$

$$X_p = R_4 = \frac{12X}{12 + X}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\frac{4}{4} = \frac{4}{\frac{12X}{12 + X}}$$

$$\therefore 12X = (48 + 4X)$$

$$\therefore 8X = 48$$

$$\therefore X = 6 \Omega$$

11. Two resistances X and Y in the two gaps of a meter-bridge give a null point dividing the wire in the ratio 2 : 3. If each resistance is increased by 30Ω , the null point divides the wire in the ratio 5 : 6, calculate each resistance.

Given :

$$\frac{X}{Y} = \frac{2}{3}$$

$$\frac{X+30}{Y+30} = \frac{5}{6}$$

To Find :

$$X = ?$$

$$Y = ?$$

Formula :

$$\frac{X}{Y} = \frac{l_x}{l_y}$$

Solution :

From 1st condition

$$\frac{X}{Y} = \frac{2}{3}$$

$$\therefore 3X = 2Y \quad \dots (i)$$

From 2nd condition

$$\frac{X+30}{Y+30} = \frac{5}{6}$$

$$\therefore 6(X+30) = 5(Y+30)$$

$$\therefore 6X + 180 = 5Y + 150$$

$$\therefore 2(3X) + 180 = 5Y + 150$$

$$\therefore 2(2Y) + 180 = 5Y + 150$$

$$\therefore 4Y + 180 = 5Y + 150$$

$$\therefore Y = 30 \Omega \quad \dots (ii)$$

From equation (i) and (ii)

$$3X = 2(30)$$

$$\therefore 3X = 60$$

$$\therefore X = 20 \Omega$$

12. Equal lengths of magnanin (ρ_1) and nichrome (ρ_2) are joined in the left gap and right gap of meter-bridge. The null point is 40 cm from the left end. Compare the diameters of the wires.

[Given : $\rho_1 = 4.8 \times 10^{-8} \Omega\text{m}$, $\rho_2 = 10^{-6} \Omega\text{m}$]

Given :

$$L_1 = L_2$$

= Lengths of magnanin and nichrome in the left and right gaps of meter bridge.

$$l_1 = 40 \text{ cm}$$

$$l_2 = 100 - 40 = 60 \text{ cm}$$

$$\rho_1 = 4.8 \times 10^{-8} \Omega\text{m}$$

$$\rho_2 = 10^{-6} \Omega\text{m}$$

To Find :

$$\frac{d_1}{d_2} = ?$$

where

$$d_1 = \text{diameter of magnanin wire}$$

$$d_2 = \text{diameter of nichrome wire}$$

Formula :

$$R = \frac{\rho L}{A}$$

Solution :

$$R = \frac{\rho L}{A}$$

$$R_1 = \rho_1 \frac{L_1}{A_1}$$

$$R_2 = \rho_2 \frac{L_2}{A_2}$$

Also

$$A_1 = \pi \frac{d_1^2}{4} \quad \text{and}$$

$$A_2 = \pi \frac{d_2^2}{4}$$

$$\therefore R_1 = \rho_1 \frac{4L_1}{\pi d_1^2} \text{ and}$$

$$R_2 = \rho_2 \frac{4L_2}{\pi d_2^2}$$

$$\therefore \frac{R_1}{R_2} = \frac{\rho_1 \left(\frac{4L_1}{\pi d_1^2} \right)}{\rho_2 \left(\frac{4L_2}{\pi d_2^2} \right)}$$

$$= \frac{\rho_1}{\rho_2} \times \frac{4L_1}{\pi d_1^2} \times \frac{\pi d_2^2}{4L_2}$$

According to balancing condition,

$$\frac{R_1}{R_2} = \frac{l_1}{l_2} = \frac{40}{60}$$

$$\therefore \frac{R_1}{R_2} = \frac{\rho_1 \left(\frac{d_2}{d_1} \right)^2}{\rho_2} \text{ becomes,}$$

$$\therefore \frac{2}{3} = \frac{4.8 \times 10^{-8}}{10^{-6}} \times \left(\frac{d_2}{d_1} \right)^2$$


$$\therefore \left(\frac{d_2}{d_1} \right)^2 = \frac{4.8 \times 10^{-8}}{10^{-6}} \times \frac{3}{2}$$

$$\therefore \left(\frac{d_1}{d_2} \right)^2 = \frac{1.44 \times 10^{-7}}{2 \times 10^{-6}}$$

$$\therefore \frac{d_1}{d_2} = \sqrt{\frac{0.144}{2}}$$

$$\therefore \frac{d_1}{d_2} = 0.2683$$

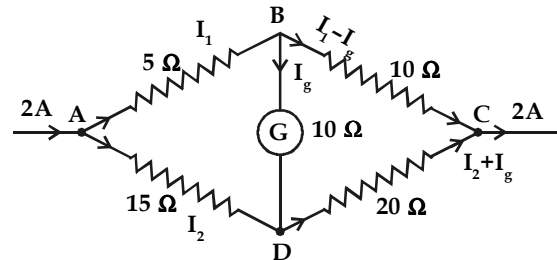13. Determine the current flowing through the galvanometer (G) as shown in the figure.



Given :

Let I_1 and I_2 be the current through AB and AD.

I_g be current through (G)

G = 10 Ω (Given)

To Find :

$$I_g = ?$$

Formula :

$$\text{i) } \Sigma I = 0$$

$$\text{ii) } \Sigma E + \Sigma IR = 0$$

Solution :

Applying Kirchhoff's 2nd law to loop ABDA

$$-5I_1 - 10I_g + 15I_2 = 0$$

$$\therefore -I_1 - 2I_g + 3I_2 = 0 \quad \dots\text{(i)}$$

Applying Kirchhoff's 2nd law to loop BCDB

$$-10(I_1 - I_g) + 20(I_2 + I_g) + 10I_g = 0$$

$$\therefore -10I_1 + 10I_g + 20I_2 + 20I_g + 10I_g = 0$$

$$\therefore -10I_1 + 20I_2 + 40I_g = 0$$

$$\therefore -I_1 + 2I_2 + 4I_g = 0 \quad \dots\text{(ii)}$$

Subtract equations (ii) and (i)

$$-I_1 + 3I_2 - 2I_g = 0$$

$$-I_1 + 2I_2 + 4I_g = 0$$

$$\begin{array}{r} + \quad - \quad - \\ \hline I_2 - 6I_g = 0 \end{array}$$

$$\therefore I_2 = 6I_g \quad \dots\text{(iii)}$$

From equations (ii) and (iii)

$$-I_1 + 2(6I_g) + 4I_g = 0$$

$$\therefore -I_1 + 12I_g + 4I_g = 0$$

$$\therefore I_1 = 16I_g \quad \dots(\text{iv})$$

Adding equations (iii) and (iv), we have

$$I_1 + I_2 = 6I_g + 16I_g$$

$$\therefore I_1 + I_2 = 22I_g$$

$$\therefore 2 = 22I_g \quad [\because I_1 + I_2 = 2]$$

$$\therefore I_g = \frac{2}{22} = \frac{1}{11}$$

$$\therefore I_g = \frac{1}{11} \text{ A}$$

Solution :

Since

$$I = \frac{E}{R + r + R_E}$$

$$\therefore K = \frac{IR}{L}$$

$$K = \frac{ER}{(R + r + R_E)L}$$

$$0.1 = \frac{2 \times 4}{(4 + 2 + R_E) \times 4}$$

$$0.1 \times (6 + R_E) = 2$$

$$6 + R_E = 20$$

$$\therefore R_E = 14 \Omega$$

14. A potentiometer wire has a length of 4Ω and resistance of 4 m . What resistance must be connected in series with the potentiometer wire and a cell of e.m.f 2 V having internal resistance 2Ω to get a potential drop of $100 \mu\text{V}/\text{mm}$ along the wire ?

Given :

$$L = 4 \text{ m}$$

$$R = 4 \Omega$$

$$E = 2 \text{ V}$$

Internal resistance of cell,

$$r = 2 \Omega$$

$$K = 100 \mu\text{V}/\text{mm}$$

$$= 100 \times 10^{-6}/10^{-3}$$

$$= 100 \times 10^{-3}$$

$$= 0.1 \text{ V}/\text{m}$$

To Find :

$$R_E = ?$$

Formula :

$$K = \frac{IR}{L}$$

$$I = \frac{E}{R + r + R_E}$$

15. A uniform wire is cut into two pieces such that one piece is twice as long as the other. The two pieces are connected in parallel in the left gap of a meter-bridge. When a resistance of 20Ω is connected in the right gap, the neutral point is obtained at a distance of 60 cm from the right end of wire. Find the resistance of the wire before it was cut into two pieces.

Given :

$$R = 20 \Omega$$

$$l_X = 40 \text{ cm}$$

$$l_R = 60 \text{ cm}$$

To Find :

$$\text{Resistance of entire wire} = ?$$

Formula :

$$X = R \cdot \frac{l_X}{l_R}$$

Solution :

Let, length of smaller piece of wire = l

$$\therefore \text{Length of larger piece of wire} = 2l$$

Correspondingly resistance of the pieces is R and $2R$.

The wires are connected parallelly in the left gap of meter bridge

$$\begin{aligned} \therefore X &= R \frac{l_x}{l_R} \\ &= 20 \times \frac{40}{60} = \frac{40}{3} \end{aligned}$$

$$\therefore X = 13.3 \Omega$$

In the left gap, equivalent resistance is given by

$$\frac{1}{X} = \frac{1}{R} + \frac{1}{2R}$$

$$\therefore \frac{1}{40} = \frac{3R}{2R^2}$$

$$\therefore \frac{3}{40} = \frac{3}{2R}$$

$$\therefore 2R = 40$$

$$\therefore R = 20 \Omega$$

Now entire resistance of wire

$$= R + 2R = 3R$$

$$= 3 \times 20 = 60 \Omega$$

16. With an unknown resistance X in the left gap and a resistance of 30 Ω in the right gap of meter-bridge, the null point is obtained at 40 cm from the left end of the wire.

Find :

- i) the unknown resistance and
- ii) the shift in the position of the null point.

a) when the resistances in both the gaps are increased by 15 Ω and

b) when the resistance in each gap is shunted by a resistance of 8 Ω.

Given :

$$R = 30 \Omega$$

$$l_x = 40 \text{ cm}$$

$$l_R = 60 \text{ cm}$$

To Find :

- i) Unknown resistance (X) = ?

ii) Shift in the position of the null point

- a) when the resistances in both the gaps are increased by 15 Ω and
- b) when the resistance in each gap is shunted by a resistance of 8 Ω.

Formula :

$$X = R \frac{l_x}{l_R}$$

Solution :

$$\text{i) } X = R \frac{l_x}{l_R}$$

$$X = 20 \times \frac{40}{60}$$

$$\therefore X = 20 \Omega$$

ii) a) When the resistance in both the gaps are increased by 15 Ω

$$X_1 = X + 15$$

$$= 20 + 15 = 35 \Omega$$

$$R_2 = R + 15$$

$$= 30 + 15 = 45 \Omega$$

$$\text{Since } l_x + l_R = 100$$

$$\therefore l_x = 100 - l_R$$

$$X = R \frac{l_x}{l_R}$$

$$35 = 45 \times \left(\frac{100 - l_R}{l_R} \right)$$

$$\therefore 35 l_R = 4500 - 45 l_R$$

$$\therefore 80 l_R = 4500$$

$$\therefore l_R = 56.25 \text{ cm}$$

$$\therefore l_x = 100 - 56.25$$

$$\therefore l_x = 43.75 \text{ cm}$$

$$\therefore \text{Shift in null point} = 43.75 - 40$$

$$\therefore \text{Shift in null point} = 3.75 \text{ cm towards right}$$

b) When the resistance in each gap is shunted by a resistance of 8 Ω new resistance in left gap

$$\frac{1}{X_2} = \frac{1}{20} + \frac{1}{8}$$

$$\therefore X_2 = \frac{8 \times 20}{8 + 20} = \frac{160}{28}$$

$$\therefore X_2 = 5.71 \Omega$$

New resistance in right gap

$$\frac{1}{R_2} = \frac{1}{30} + \frac{1}{8}$$

$$\therefore R_2 = \frac{30 \times 8}{30 + 8} = \frac{240}{38}$$

$$\therefore R_2 = 6.31 \Omega$$

$$X_2 = R_2 \cdot \frac{l_x}{l_R}$$

$$5.71 = 6.31 \times \left(\frac{100 - l_R}{l_R} \right)$$

$$0.905 = \frac{100 - l_R}{l_R}$$

$$0.905 l_R = 100 - l_R$$

$$1.905 l_R = 100$$

$$l_R = 52.5$$

$$\therefore l_x = 100 - 52.5 = 47.5 \text{ cm}$$

$$\therefore l_x = 47.5 \text{ cm}$$


$$\therefore \text{shift in null point} = 47.5 - 40$$

$$\therefore \text{shift in null point} = 7.5 \text{ cm towards right}$$

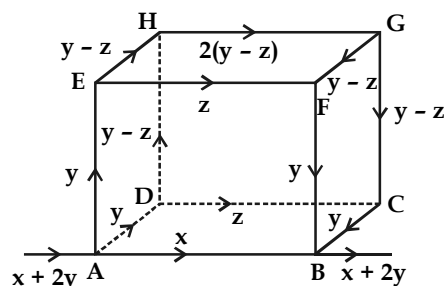17. A skeleton cube is made of 12 wires each of resistance $r\Omega$ connected to a cell of e.m.f. E and of negligible internal resistance. Use Kirchhoff's laws to find the resistance between
- adjacent corners of the cube i.e. between two ends of any wire across any one edge.
 - the diagonally opposite corners of same face of cube. i.e. across face diagonal.

Solution :

Let a current $x + 2y$ enter the junction A of the cube ABCDEFGH. From the symmetry of the parallel paths, current distribution will be as shown in figure.



Applying Kirchoff's second law to the loop DHGCD, we get

$$(y - z) r + 2(y - z) r + (y - z)r - zr = 0$$

$$\therefore 4y r - 5z r = 0$$

$$\therefore 5z = 4y$$

$$\therefore z = \frac{4}{5} y$$

Applying Kirchoff's second law to the loop ABCDA, we get

$$xr - yr - zr - yr = 0 \text{ or } x - 2y - z = 0$$

$$\therefore x - 2y - \frac{4}{5} y = 0 \left(\because z = \frac{4}{5} y \right)$$

$$\therefore x = \frac{14}{5} y;$$

$$y = \frac{5}{14} x$$

Let R be the resistance across AB. Then P.D. across AB = xr

$$\text{i.e., } (x + 2y) R = xr$$

$$\therefore \left(x + \frac{10}{14} x \right) R = xr$$

$$\therefore \frac{12}{7} R = r$$

$$\therefore R = \frac{7}{12} r \Omega$$

Let R be the resistance across AC (i.e. opposite corners of the loop ADCBA)

$$\text{P.D. across AC} = V_{AD} + V_{DC}$$

$$\therefore (x + 2y)R = (y + z)r$$

$$\therefore \left(\frac{14}{5}y + 2y\right)R = \left(y + \frac{4}{5}y\right)r$$

$$\therefore \frac{24}{5}yR = \frac{9yr}{5}$$

$$\therefore R = \frac{9}{24}r$$

$$\therefore R = \frac{3}{8} r \Omega$$

18. Two coils are connected in series in one gap of meter-bridge and null point is obtained at the middle of the wire by putting 50 Ω resistance in the other gap. The two coils are then connected in parallel and it is found that the resistance in the other gap has to be decreased by 38 Ω to get the null point at the same place as before. Find the resistance of the coils.

Solution :

Let R_1 and R_2 be the resistance of two coils.

Equivalent resistance in series

$$R_s = (R_1 + R_2)$$

From first condition

$$\frac{R_1 + R_2}{50} = \frac{50}{50}$$

$$\therefore R_1 + R_2 = 50 \quad \dots(i)$$

From second condition

R_1 and R_2 are in parallel

\therefore Equivalent resistance

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R_p = \frac{R_1 R_2}{R_1 + R_2}$$

Resistance in other gap = $50 - 38 = 12 \Omega$
 Since null point remains at mid point

$$\therefore \frac{R_p}{12} = \frac{50}{50}$$

$$\therefore \frac{R_1 R_2}{R_1 + R_2} = 12$$

Using equation (i) $R_1 R_2 = 50 \times 12$

$$\therefore R_2 = \frac{50 \times 12}{R_1}$$

Substituting R_2 in equation (i) we have

$$R_1 + \frac{50 \times 12}{R_1} = 50$$

$$\therefore R_1^2 - 50 R_1 + 600 = 0$$

$$\therefore R_1^2 - 20 R_1 - 30 R_1 + 600 = 0$$

$$\therefore R_1 (R_1 - 20) - 30(R_1 - 20) = 0$$

$$\therefore (R_1 - 20)(R_1 - 30) = 0$$

Either

$$R_1 - 20 = 0 \quad \text{or} \quad R_1 - 30 = 0$$

If $R_1 = 20 \Omega$, If $R_1 = 30 \Omega$
 then $R_2 = 30 \Omega$ Then, $R_2 = 20 \Omega$

19. Find the radius of the wire of length 25 m needed to prepare a coil of resistance 25 Ω (Restivity of material of wire is $3.142 \times 10^{-7} \Omega m$)

Given :

$$L = 25 \text{ m}$$

$$R = 25 \Omega$$

$$\rho = 3.142 \times 10^{-7} \Omega m$$

To Find :

$$r = ?$$

Formula :

$$R = \frac{\rho L}{A}$$

Solution :

$$R = \frac{\rho L}{A}$$

$$R = \frac{\rho L}{\pi r^2}$$

$$25 = \frac{3.142 \times 10^{-7} \times 25}{3.142 \times r^2}$$

$$\therefore r^2 = 10^{-7}$$

$$\begin{aligned} \therefore r &= 0.3162 \times 10^{-3} \text{ m} \\ &= 0.3162 \text{ mm} \end{aligned}$$

$$K = \frac{ER}{(R + R_E)L}$$

$$R + R_E = \frac{ER}{KL}$$

$$\therefore R_E = \frac{2 \times 8}{10^{-3} \times 8} - 8$$

$$\therefore R_E = 2000 - 8$$

$$\therefore R_E = 1992 \Omega$$

20. The resistance of a potentiometer wire is 8Ω and its length is 8 m. A resistance box and a 2V battery are connected in series with it. What should be the resistance in the box, if it is desired to have potential drop of $1 \mu\text{V}/\text{mm}$?

Given :

$$R = 8 \Omega$$

$$L = 8 \text{ m}$$

$$E = 2 \text{ V}$$

$$K = 1 \mu\text{V}/\text{mm}$$

$$= 1 \times \left(\frac{10^{-6}}{10^{-3}} \right) \text{ V/m}$$

$$= 10^{-3} \text{ V/m}$$

To Find :

$$R_E = ?$$

Formula :

$$K = \frac{V}{L}$$

Solution :

Since,

$$I = \frac{E}{R + R_E}$$

Also

$$V = IR = \frac{ER}{R + R_E}$$

$$\therefore K = \frac{V}{L} \text{ becomes,}$$