

14. MAGNETIC EFFECT OF ELECTRIC CURRENT

1. A rectangular coil in a moving galvanometer has 50 turns each of length 5 cm and breadth 3 cm, which is suspended in a radial magnetic field of 0.050 Wb/m^2 . The twist constant of suspension is $1.5 \times 10^{-9} \text{ Nm/deg}$. Calculate the current through the coil which will deflect it through 30° .

Given :

$$\begin{aligned} n &= 50 \\ C &= 1.5 \times 10^{-9} \text{ Nm/deg} \\ B &= 0.05 \text{ Wb/m}^2 \\ \theta &= 30^\circ \\ A &= l \times b = 5 \times 3 \\ &= 15 \text{ cm}^2 \\ &= 15 \times 10^{-4} \text{ m}^2 \end{aligned}$$

To Find :

$$I = ?$$

Formula :

$$I = \frac{c\theta}{nAB}$$

Solution :

$$I = \frac{c\theta}{nAB}$$

$$I = \frac{1.5 \times 10^{-9} \times 30}{50 \times 15 \times 10^{-4} \times 0.05}$$

$$\therefore I = 1.2 \times 10^{-5} \text{ A}$$

2. A galvanometer with a coil of resistance 40 ohm gives a full scale deflection for a current of 5 mA. How will you convert it into an ammeter of range 0-5 A ?

Given :

$$\begin{aligned} G &= 40 \ \Omega \\ I_g &= 5 \text{ mA} \\ &= 5 \times 10^{-3} \text{ A} \\ I &= 5 \text{ A} \end{aligned}$$

To Find :

$$S = ?$$

Formula :

$$S = \left(\frac{I_g}{I - I_g} \right) G$$

Solution :

$$S = \left(\frac{I_g}{I - I_g} \right) G$$

$$S = \left(\frac{5 \times 10^{-3}}{5 - 5 \times 10^{-3}} \right) \times 40$$

$$= 0.04 \ \Omega$$

$$\therefore S = 0.04 \ \Omega$$

\therefore A shunt of $0.04 \ \Omega$ is to be connected in parallel with galvanometer (convert if in to am meter of range 0 - 5 A).

3. Calculate the value of resistance needed to convert a moving coil galvanometer of $60 \ \Omega$ into an ammeter of range 5 A which gives full scale deflection for a current of 50 mA and into voltmeter of range 0 - 50 V.

Given :

$$\begin{aligned} G &= 60 \ \Omega \\ V &= 50 \text{ V} \\ I &= 5 \text{ A} \\ I_g &= 50 \text{ mA} = 50 \times 10^{-3} \text{ A} \\ &= 5 \times 10^{-2} \text{ A} \end{aligned}$$

To Find :

$$\text{i) } R_s = ?$$

Formula :

$$\text{i) } R_s = \frac{V}{I_g} - G$$

$$\text{ii) } S = \frac{GI_g}{I - I_g}$$

Solution :

$$R_s = \frac{V}{I_g} - G$$

$$R_s = \frac{50}{5 \times 10^{-2}} - 60$$

$$\therefore R_s = 1000 - 60$$

$$\therefore R_s = 940 \Omega$$

$$S = \frac{GI_g}{I - I_g}$$

$$S = \frac{60 \times 0.05}{5 - 0.05}$$

$$= \frac{3}{4.95}$$

$$\therefore S = 0.6061 \Omega$$


\therefore A resistance of 0.6061Ω in parallel and 940Ω in series is connected to M.C.G.

4. A galvanometer has a resistance of 16Ω and gives a full scale deflection when a current of 20 mA is passed through it. The only shunt resistance available is 0.04Ω which is not appropriate to convert galvanometer into an ammeter. How much resistance should be connected in series with coil of galvanometer so that the range of ammeter is 10 A ?

Solution :

Let 'X' be the resistance connected in series with galvanometer.

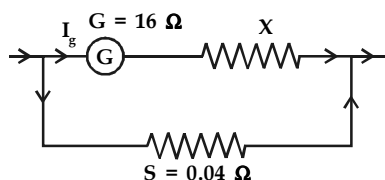Since S is not sufficient for $I = 10 \text{ A}$
 $G = 16 \Omega$,



\therefore From the figure,

$$\frac{I_g}{I} = \frac{S}{(G+X)+S}$$

Magnetic Effect of Electric Current

$$\therefore (G + X) + S = \frac{I}{I_g} S$$

$$\therefore (16 + X + 0.04) = \frac{10}{2 \times 10^{-2}} \times 0.04$$

$$\therefore (16 + X + 0.04) = 20$$

$$\therefore X = 20 - 16.04$$

$$\therefore X = 3.96 \Omega$$

5. A resistance of 3 ohm is connected in parallel to a galvanometer of resistance 297 ohm . Find the fraction of current passing through galvanometer.

Given :

$$S = 3 \Omega$$

$$G = 297 \Omega$$

To Find :

$$\frac{I_g}{I} = ?$$

Formula :

$$I_g G = (I - I_g) S$$

Solution :

$$I_g G = (I - I_g) S$$

$$\therefore \frac{G}{S} + 1 = \frac{I}{I_g}$$

$$\therefore \frac{G+S}{S} = \frac{I}{I_g}$$

$$\therefore \frac{I_g}{I} = \frac{S}{G+S} = \frac{3}{297+3}$$

$$\therefore \frac{I_g}{I} = \frac{3}{300} = \left[\frac{3}{300} \times 100 \right]$$

$$\therefore \frac{I_g}{I} = 0.01 \text{ or } 1 \%$$

6. The combined resistance of galvanometer of resistance 1000 ohm and its shunt is 25 ohm . Calculate the value of shunt.

Given :

$$G = 1000 \Omega$$

$$R_{eq} = 25 \Omega$$

To Find :

$$S = ?$$

Formula :

$$\frac{1}{R_{eq}} = \frac{1}{G} + \frac{1}{S}$$

Solution :

$$\frac{1}{R_{eq}} = \frac{1}{G} + \frac{1}{S}$$

$$\frac{1}{S} = \frac{1}{R_{eq}} - \frac{1}{G} = \frac{G - R_{eq}}{R_{eq} G}$$

$$\therefore S = \frac{R_{eq} G}{G - R_{eq}}$$

$$\therefore S = \frac{25 \times 1000}{1000 - 25}$$

$$= \frac{25 \times 1000}{975}$$

$$\therefore S = 25.64 \Omega$$

7. A rectangular coil of moving coil galvanometer contains 50 turns each having area 12 cm². It is suspended in radial magnetic field of induction 0.025 Wb/m² by a fibre of twist constant 15 × 10⁻¹⁰ Nm/deg. Calculate the sensitivity of a moving coil galvanometer.

Given :

$$n = 50$$

$$A = 12 \text{ cm}^2$$

$$= 12 \times 10^{-4} \text{ m}^2$$

$$B = 0.025 \text{ Wb/m}^2$$

$$c = 15 \times 10^{-10} \text{ Nm/deg}$$

To Find :

$$S_i = ?$$

Formula :

$$S_i = \frac{nAB}{c}$$

Solution :

Current sensitivity of MCG

$$S_i = \frac{nAB}{c}$$

$$S_i = \frac{50 \times 12 \times 10^{-4} \times 0.025}{15 \times 10^{-10}}$$

$$\therefore S_i = 10^6 \text{ deg/A}$$