

11. CURRENT ELECTRICITY

HOMework SOLUTION

1. Given :

$$V = 240 \text{ V}$$

$$I = 0.25 \text{ A}$$

$$t = 10 \text{ sec}$$

To Find :

$$R = ?$$

$$q = ?$$

Formulae :

$$\text{i) } V = IR$$

$$\text{ii) } I = \frac{q}{t}$$

Solution :

$$V = IR$$

$$240 = 0.25 \times R$$

$$\therefore R = \frac{240}{0.25}$$

$$\therefore R = 960 \Omega$$

$$I = \frac{q}{t}$$

$$q = It$$

$$= 0.25 \times 10$$

$$q = 2.5 \text{ C}$$

2. Given :

$$l_1 = 2.4 \text{ m}$$

$$R_1 = 10 \Omega$$

$$l_2 = 1.2 \text{ m}$$

To Find :

$$R_2 = ?$$

Formulae :

$$R = \rho \frac{l}{A}$$

Solution :

$$R_1 = \rho \frac{l_1}{A} \quad \dots \text{ (i)}$$

$$R_2 = \rho \frac{l_2}{A} \quad \dots \text{ (ii)}$$

(Here, the wire is of the same material and same cross sectional area)

Dividing equation (i) , (ii), we get,

$$\frac{R_1}{R_2} = \frac{l_1}{l_2}$$

$$\frac{10}{R_2} = \frac{2.4}{1.2}$$

$$\therefore R_2 = \frac{10 \times 1.2}{2.4}$$

$$R_2 = 5 \Omega$$

3. Given :

Original resistance (R_1) = R

Original length (l_1) = X

Final length (l_2) = nX

To Find :

Final resistance (R_2) = ?

Formulae :

$$R = \rho \frac{l}{A}$$

Solution :

Let A_1 and A_2 be original area and final area. After wire is stretched length increases and area decreases.

But volume remains constant

$$V_1 = V_2$$

$$A_1 l_1 = A_2 l_2$$

$$A_1 (X) = A_2 (nX)$$

$$A_1 = nA_2$$

$$R_1 = \rho \frac{l_1}{A_1} \quad R_2 = \rho \frac{l_2}{A_2}$$

$$\frac{R_2}{R_1} = \frac{l_2}{A_2} \times \frac{A_1}{l_1}$$

$$= \frac{nX}{A_2} \times \frac{nA_2}{X}$$

$$= n^2$$

$$R_2 = n^2 R_1$$
 Final resistance is n^2 times the original resistance.

4. Given :

Original resistance (R_1) = R
 Original length (l_1) = 0.01 m
 Original area (A_1) = (0.01) [\because cube]
 Final length (l_2) = 2m
 Final area (A_2) = (2)²
 $\rho = 0.55 \times 10^{-6} \Omega\text{m}$

To Find :

Final resistance (R_2) = ?

Formulae :

$$R = \rho \frac{l}{A}$$

Solution :

$$R_1 = \rho \frac{l_1}{A_1} \quad \frac{l_1}{l_1^2} = \frac{\rho}{l_1}$$

$$R_1 = \frac{0.55 \times 10^{-6} \times 0.01}{(0.01)^2}$$

$$= \frac{0.55 \times 10^{-6}}{0.01}$$

$$R_1 = 0.55 \times 10^{-4}$$

Now $R \propto l$

Let A_1 and A_2 be the original area and final area.
 Since the volume of wire remains the same.

$$l_1 A_1 = l_2 A_2$$

$$\therefore \frac{A_2}{A_1} = \frac{l_1}{l_2}$$

$$\therefore \frac{R_1}{R_2} = \left(\frac{l_1}{l_2} \right)^2$$

$$\therefore \frac{0.55 \times 10^{-4}}{R_2} = \frac{(0.01)^2}{4}$$

$$R_2 = 2.2 \Omega$$

5. Given :

Original resistance (R_1) = 8 Ω

Original length (l_1) = x

Final length (l_2) = $\frac{x}{2}$

To Find :

Final resistance (R_2) = ?

Formulae :

$$R = \rho \frac{l}{A}$$

Solution :

$$R_1 = \rho \frac{l_1}{A_1}$$

$$R_2 = \rho \frac{l_2}{A_2}$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{A_2}{A_1} \quad \dots (i)$$

Since the volume of wire remains the same in two cases.

$$l_1 A_1 = l_2 A_2$$

$$\therefore \frac{A_2}{A_1} = \frac{l_1}{l_2}$$

Substituting this in equation (i),

$$\therefore \frac{R_1}{R_2} = \left(\frac{l_1}{l_2} \right)^2$$

$$\therefore \frac{8}{R_2} = 4$$

$$\therefore R_2 = \frac{8}{4} = 2 \Omega$$

$$\therefore R_2 = 2 \Omega$$

6. Given :

$l = 50 \text{ cm} = 0.5 \text{ m}$

$b = 2 \text{ cm} = 2 \times 10^{-2} \text{ m}$

$h = 1 \text{ cm} = 10^{-2} \text{ m}$

$\rho = 6 \times 10^{-6} \Omega\text{m}$

Solution :

$$A = b \times h$$

$$A = (2 \times 10^{-2}) \times (10^{-2})$$

$$= 2 \times 10^{-4} \text{ m}$$

$$R = \rho \frac{l}{A}$$

$$= \frac{0.5 \times 6 \times 10^{-6}}{2 \times 10^{-4}}$$

$$R = 0.015 \Omega$$

7.

Brown	Black	Orange	Gold	
↓	↓	↓	↓	ohm
1	0	10 ³	5%	

$$\therefore 10000 \Omega \pm 5 \%$$

$$10 \text{ K } \Omega \pm 5 \%$$

8. Given :

$$r = 6 \Omega$$

$$R_1 = 14 \Omega$$

$$I_1 = 0.5 \text{ A}$$

$$R_2 = 24 \Omega$$

To Find :

$$I_2 = ?$$

Formulae :

$$I = \frac{E}{R + r}$$

Solution :

$$I_1 = \frac{E}{R_1 + r}$$

$$0.5 = \frac{E}{14 + 6}$$

$$0.5 = \frac{E}{20}$$

$$\therefore E = 0.5 \times 20$$

$$\therefore E = 10 \text{ V}$$

$$I_2 = \frac{E}{R_2 + r}$$

$$= \frac{10}{24 + 6} = \frac{10}{30}$$


$$I_2 = \frac{1}{3} \text{ A}$$

9. Given :

Let the 3 equal resistors be of $R \Omega$

When connected in series

$$R_s = R + R + R = 3R$$

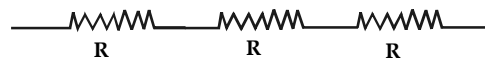


$$P_s = 10 \text{ W}$$

When connected in parallel

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$

$$\therefore R_p = \frac{R}{3}$$

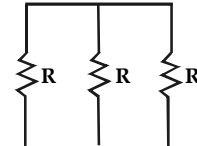

To Find :

$$P_p = ?$$

Solution :

$$P = \frac{V^2}{R}$$

$$P_s = \frac{V^2}{R_s} \quad \text{and} \quad P_p = \frac{V^2}{R_p}$$

$$\frac{P_s}{P_p} = \frac{R_p}{R_s}$$

$$\therefore \frac{10}{P_p} = \frac{R}{3.3R}$$

$$\frac{10}{P_p} = \frac{1}{9}$$

$$P_p = 90 \text{ W}$$

10. Given :

$$Q = 3C$$

$$V_1 = 120V \quad V_2 = 200V$$

To Find :

$$W = ?$$

Formulae :

$$W = QV$$

Solution :

$$W = Q(V_2 - V_1)$$

$$W = 3 \times (200 - 120)$$

$$W = 3 \times 80$$

$$W = 240J$$

11. Given :

$$\text{Resistance of wire} = 2.1 \Omega (R_0)$$

$$T = 100^\circ\text{C} - 27.5^\circ\text{C}$$

$$T = 72.5^\circ\text{C}$$

$$\alpha = 3.94 \times 10^{-3}/^\circ\text{C}$$

To Find :

$$R_T = ?$$

Formulae :

$$\alpha = \frac{R_T - R_0}{R_0 T}$$

Solution :

$$3.94 \times 10^{-3} = \frac{R_T - 2.1}{152.25}$$

$$3.94 \times 10^{-3} \times 152.25 = R_T - 2.1$$

$$3.94 \times 10^{-5} \times 152.25 = R_T - 2.1$$

$$AI \left[\begin{array}{l} \log 394 \\ + \log 152.25 \end{array} \right] \times 10^{-5} = R_T - 2.1$$

$$AI [2.5955 + 2.1824] \times 10^{-5} = R_T - 2.1$$

$$AI [4.7779] \times 10^{-5} = R_T - 2.1$$

$$5.996 \times 10^4 \times 10^{-5} = R_T - 2.1$$

$$5.996 \times 10^{-1} = R_T - 2.1$$

$$0.5996 = R_T - 2.1$$

$$R_T = 2.699\Omega$$

12. Given :

$$R_1 + R_2 = 18 \Omega$$

$$R_1 || R_2 = 4 \Omega$$

To Find :

$$R_1, R_2 = ?$$

Solution :

Let the two resistances be R_1 and R_2 . When connected in series

$$R_1 + R_2 = 18 \quad \dots (i)$$

When connected in parallel

$$\frac{R_1 R_2}{R_1 + R_2} = 4 \quad \dots (ii)$$

$$\therefore \frac{R_1 R_2}{18} = 4 \quad (\text{From (i)})$$

$$\therefore R_1 R_2 = 72$$

$$R_1 (18 - R_1) = 72$$

$$18R_1 - R_1^2 = 72$$

$$R_1^2 - 18R_1 + 72 = 0$$

$$R_1^2 - 6R_1 - 12R_1 + 72 = 0$$

$$R_1 (R_1 - 6) - 12 (R_1 - 6) = 0$$


$$(R_1 - 12) (R_1 - 6) = 0$$

$$R_1 = 6\Omega \quad \text{to} \quad R_1 = 12\Omega$$

$$\text{When } R_1 = 6\Omega, 6 + R_2 = 18 \quad R_2 = 12\Omega$$

$$\text{When } R_1 = 12\Omega, 12 + R_2 = 18 \quad R_2 = 6\Omega$$


The two resistances are 6Ω and 12Ω

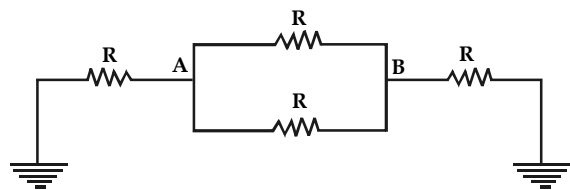13. Given :**To Find :**

$$R_{AB} = ?$$

Solution :

The circuit can be redrawn as follows :

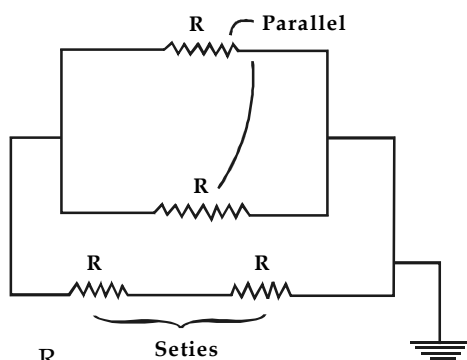

$$\frac{R}{2} \parallel 2R$$

$$= \frac{\frac{R}{2} \times 2R}{\frac{R}{2} + 2R}$$

$$= \frac{R^2}{\frac{5}{2} R}$$

$$R_{AB} = \frac{2}{5} R$$

14. Given :

$$I_1 : I_2 : I_3 = 2 : 3 : 5$$

$$I_1 + I_2 + I_3 = 31 \text{ A}$$

To Find :

$$I_1, I_2, I_3 = ?$$

Solution :

$$R = \rho \frac{l}{A}$$

$$R \propto l$$

$$\therefore I_1 : I_2 : I_3 = R_1 : R_2 : R_3 = 2 : 3 : 5$$

Now, $I_1 + I_2 + I_3 = 31$

(I)

$$I_1 R_1 = I_2 R_2$$

$$I_1 \times \frac{R_1}{R_2} = I_2$$

$$I_1 \times \frac{2}{3} = I_2$$

(II)

$$I_1 R_1 = I_3 R_3$$

$$I_1 \times \frac{R_1}{R_3} = I_3$$

$$I_1 \times \frac{2}{5} = I_3$$

Substituting in equation (i), we get

$$I_1 + \frac{2}{3} I_1 + \frac{2}{5} I_1 = 31$$

$$\frac{15I_1}{15} + \frac{10I_1}{15} + \frac{6I_1}{15} = 31$$

$$\therefore \frac{31I_1}{15} = 31$$

$$\therefore I_1 = 15 \text{ A}$$

$$I_2 = I_1 \times \frac{2}{3} = 15 \times \frac{2}{3} = 10 \text{ A}$$

$$I_3 = I_1 \times \frac{2}{5} = 15 \times \frac{2}{5} = 6 \text{ A}$$

15. Given :


Two cells of 2V/500mA connected in parallel

To Find :

Total output voltage = ?

Current capacity = ?

Solution :

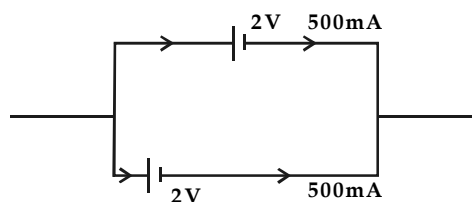

Total output voltage = 2V

(∵ the cells are connected in parallel)

$$\begin{aligned} \text{Total output current} &= 500\text{mA} + 500\text{mA} \\ &= 1000\text{mA} \\ &= 1\text{A} \end{aligned}$$

16. Given :

Power = 250 watt
Daily usage = 8 hrs/day
Total Period = 30 days
Rate = Rs3/kWh

To Find :

cost of electrical energy = ?

Solution :

Electric energy consumed per day

$$E = 250 \times 8 = 2000 \text{ watt day}$$

Electric energy consumed in 30 days

$$E_1 = 2000 \text{ watt/day} \times 30 \text{ day}$$

$$= 60000 \text{ watt}$$

$$= 60 \text{ kWh}$$

Hence, total cost is given as

$$\text{cost} = \text{Rs}3/\text{kWh} \times 60 \text{ kWh}$$

$$\text{cost} = \text{Rs}180$$