

XII – PHYSICS SOLUTIONS

Q.1 [D]

Sol. Since, $\cos\theta = \frac{R}{Z} = \frac{IR}{IZ} = \frac{8}{10} = \frac{4}{5}$

($\cos\theta$ can never be greater than 1)

Also, $I_{X_C} > I_{X_L} \Rightarrow X_C > X_L$

Current will be leading

In a LCR circuit

$$V = \sqrt{(V_L - V_C)^2 + R^2} = \sqrt{(6-12)^2 + 8^2}$$

$V = 10$; which is less than voltage drop across capacitor .

Q.2 [D]

Sol. $V(t) = -V_0 + \frac{2V_0}{T} \times t$

$$V_{\text{rms}} = \sqrt{\frac{\int_0^T V^2 dt}{\int_0^T dt}}$$


$$\sqrt{\frac{\int_0^T \left(V_0^2 + \frac{4V_0^2 t^2}{T^2} - \frac{4V_0^2 t}{T} \right) dt}{\int_0^T dt}}$$

$$\sqrt{\frac{V_0^2 T + \frac{4V_0^2 T}{3} - 2V_0^2 T}{T}} = \frac{V_0}{3}$$

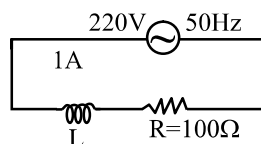Q.3 [D]

Sol. From the rating of the bulb, the resistance of the bulb can be calculated.

$$R = \frac{V_{\text{rms}}^2}{P} = 100\Omega$$



For the full to be operated at its rated value the rms current through it should be 1A

Also,

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} \therefore 1 = \frac{200}{\sqrt{100^2 + (2\pi 50L)^2}} \Rightarrow L = \frac{\sqrt{3}}{\pi} \text{ H}$$

Q.4 [B]

Sol. $V_{\text{source}} = \sqrt{V_R^2 + V_C^2}$
 $\therefore V_C = \sqrt{V_{\text{Source}}^2 - V_R^2}$
 $= \sqrt{(20)^2 - (12)^2}$
 $= 16 \text{ V}$

Q.5 [D]


Sol. $i_0 = \frac{V_0}{Z}$,
 $Z = \sqrt{R^2 + (\omega L)^2}$
 $= \sqrt{4^2 + (1000 \times 3 \times 10^{-3})^2} = 5 \Omega$
 $i_0 = \frac{4}{5}$
 $i_0 = 0.8 \text{ A}$

Q.6 [A]

Sol. From Kirchoff's current law,
 $i_3 = i_1 + i_2 = 3 \sin \omega t + 4 \sin (\omega t + 90^\circ)$
 $= \sqrt{3^2 + 4^2 + 2(3)(4) \cos 90^\circ} \sin(\omega t + \phi)$
 where $\tan \phi = \frac{4 \sin 90^\circ}{3 + 4 \cos 90^\circ} = \frac{4}{3}$
 $\therefore i_3 = 5 \sin(\omega t + 53^\circ)$

Q.7 [D]

Sol.

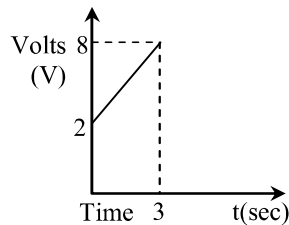

$$I = \frac{dq}{dt}$$

$$q = it + a$$

$$V = \frac{q}{c}$$

$$V = \frac{it + a}{c}$$

$\therefore V$ is proportional to time.

Q.8 [B]

Sol. $P = V_{\text{rms}} I_{\text{rms}} \cos\phi$

$$P = V_{\text{rms}} \frac{V_{\text{rms}}}{Z} \frac{R}{Z}$$

$$= \frac{V_{\text{rms}}^2}{Z^2} R$$

$$Z = \sqrt{R^2 + (L\omega)^2} = \sqrt{(50)^2 + (0.2 \times 250)^2}$$

$$= \sqrt{2500 + (50)^2} = 50\sqrt{2}$$

$$\therefore P = \left(\frac{200}{\sqrt{2}}\right)^2 \times \frac{50}{50\sqrt{2}} \times \frac{1}{50\sqrt{2}}$$

$$= 200 \text{ watt}$$

Q.9 [A]

Sol. $X_C = \frac{1}{C\omega} = \frac{1}{20 \times 10^{-6} \times 2\pi \times \frac{50}{\pi}} = 500 \Omega$

$$X_L = L\omega = L \times 2\pi \times \frac{50}{\pi} = 100 \Omega$$

$$I_{\text{rms}} = \frac{E_{\text{rms}}}{2} = \frac{50}{\sqrt{R^2 + (X_C - X_L)^2}}$$

$$= \frac{50}{\sqrt{(300)^2 + (500 - 100)^2}}$$

$$= \frac{50}{500} = \frac{1}{10} \text{ A}$$

$$V_C = I_{\text{rms}} \times X_C$$

$$= \frac{1}{10} \times 500 \text{ V}$$

$$= 50 \text{ V}$$

Q.10 [C]

Sol. As we know, that alternating volts leads the alternating current by a phase angle of 90° in an inductance coil. Therefore the answer is (C).

Q.11 [D]

Sol. When capacitance is removed

$$\tan \theta = \frac{\omega L}{R} \text{ or } \omega L = 100 \tan 60^\circ \quad \dots(1)$$

when inductance is removed

$$\tan \phi = \frac{1}{(\omega C)(R)} \text{ or } \frac{1}{\omega C} = 100 \tan 60^\circ \quad \dots(2)$$

$$\text{So } Z = R = 100 \Omega$$

$$I = V/R = 200/100 = 2 \text{ A}$$

$$\text{Power } P = I^2 R = 4 \times 100 = 400 \text{ W}$$

Q.12 [C]

Sol. $E_0 = 200\sqrt{2} \text{ V}$ and $\omega = 100 \text{ rad./s}$

$$\text{So } X_c = \frac{1}{\omega c} = \frac{1}{100 \times 10^{-6}} = 10^4 \Omega$$

As ammeter reads rms value of current

$$\begin{aligned} \therefore I_{\text{rms}} &= \frac{E_{\text{rms}}}{Z} = \frac{E_0}{(\sqrt{2})X_c} \\ &= \frac{200\sqrt{2}}{\sqrt{2} \times 10^4} \\ &= 20 \text{ mA} \end{aligned}$$

Q.13 [A]

Sol. $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$\text{Here } X_L = 2\pi fL = 2 \times 3.14 \times 500 \times (8.1 \times 10^{-3}) = 25.4 \Omega$$

$$\text{and } X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 500 \times 12.5 \times 10^{-6}} = 25.4 \Omega$$

$$\therefore Z = \sqrt{(10)^2 + (25.4 - 25.4)^2} = 10 \Omega$$

$$\text{Now } i_{\text{rms}} = \frac{E_{\text{rms}}}{Z} = \frac{100}{10} = 10 \text{ A}$$

$$\begin{aligned} \therefore V_R &= i_{\text{rms}} \times R \\ &= 10 \times 10 \\ &= 100 \text{ V} \end{aligned}$$

Q.14 [C]

Sol. $P = V_{\text{rms}} I_{\text{rms}} \cos \phi$

$$= \left(\frac{100}{\sqrt{2}}\right) \left(\frac{100}{\sqrt{2}}\right) \times 10^{-3} \cos \frac{\pi}{3}$$

$$= 2.5 \text{ W}$$

Q.15 [C]

Sol. % efficiency = $\frac{P_{\text{out}}}{P_{\text{in}}} \times 100 = \frac{110 \times 9}{220 \times 5} \times 100 = 90\%$

Q.16 [A]

Sol. $L = 10 \text{ mHz} = 10^{-2} \text{ Hz}$, $f = 1 \text{ MHz} = 10^6 \text{ Hz}$

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow f^2 = \frac{1}{4\pi^2 LC} \Rightarrow C = \frac{1}{4\pi^2 f^2 L}$$

$$= \frac{1}{4 \times 10 \times 10^{-2} \times 10^{12}} = \frac{10^{-12}}{4} = 2.5 \text{ pF}$$

Q.17 [D]

Sol. Use $P_{av} = \left(\frac{V_{rms}}{Z} \right)^2 R$

Q.18 [C]

Sol. Use $\frac{V_s}{V_p} = \frac{N_s}{N_p}$ Frequency in transformer remains same.

Q.19 [A]

Sol. $i = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X_c^2}} = \frac{V}{\sqrt{R^2 + (1/\omega C)^2}}$

Q.20 [B]

Sol. Let ϕ is the phase difference between V and i

$$\tan \phi = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{100 \times 1}{100} = \frac{\pi}{4}$$

From diagram it is clear that i lags with V
 \therefore Instantaneous current equation will be

$$i_0 = \sin(100t - \phi) \text{ where } \phi = \frac{\pi}{4} \text{ and } i_0 = \frac{V_0}{Z}$$

$$= \frac{V_0}{\sqrt{R^2 + (\omega L)^2}} = \frac{200}{\sqrt{(100)^2 + (100 \times 1)^2}} = \sqrt{2}$$

$$\therefore i = \sqrt{2} \sin(100t - \frac{\pi}{4})$$

Q.21 [A]

Sol. $E = 10 \sin(20t + \phi)$

$$\tan \phi = \frac{8}{6}$$

$$i = \frac{10}{\sqrt{2}R} = \frac{10}{R} = \frac{2 \text{ amp}}{\sqrt{2}}$$

$$\text{Power dissipated} = i^2 R = \frac{4 \times 5}{2}$$



$$= 10 \text{ watt}$$

$$\therefore C = \frac{1}{\omega^2 L} = \frac{1}{400 \times 0.2}$$

$$= 12.5 \text{ Mf}$$

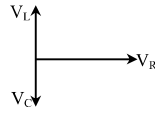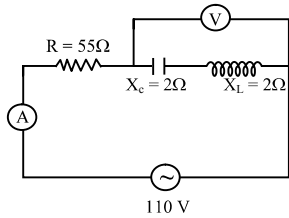Q.22 [B]

Sol. The circuit is RLC resonant circuit.



$$\therefore \text{Reading of voltmeter} = V_L - V_C = 0$$

$$\text{Reading of ammeter} = \frac{E_{\text{rms}}}{Z} = \frac{E_{\text{rms}}}{R} = \frac{110}{55} = 2\text{A}$$

Q.23 [D]

Sol.

$$V_R^2 + (V_L - V_C)^2 = E_{\text{rms}}^2$$

$$(V_L - V_C)^2 = (500)^2 - (400)^2$$

$$V_L - V_C = \sqrt{(500)^2 - (400)^2} = 300$$

$$V_C = V_L - 300 = 700 - 300 = 400$$

$$\therefore V_C(\text{peak}) = \sqrt{2} V_C = \sqrt{2} \times 400 \text{ volts}$$

Q.24 [D]

Sol. $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Q.25 [D]

Sol. $\frac{V_0}{\sqrt{2}} = V_0 \sin(\omega t)$

$$\frac{2\pi}{T} \times t = \frac{\pi}{4} \Rightarrow t_1 = \frac{7}{8} T$$

Time taken to reach the peak is $\frac{T}{4}$

$$\therefore \text{interval} = \frac{T}{4} - \frac{T}{8} = \frac{T}{8} = \frac{1}{8f} = \frac{1}{8 \times 50}$$

$$= \frac{1}{400} = 2.5 \times 10^{-3} \text{ sec.}$$

Q.26 [D]

Sol. $I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{240}{30} = 8\text{A}$

Reading of voltmeter is zero.

Q.27 [A]

Sol. At resonance $V_{\text{net}} = V_R \Rightarrow V_3 = V_1$

Q.28 [A]

Sol. $Z = \sqrt{3^2 + (15 - 11)^2} = 5$

$$\therefore I = \frac{V}{Z} = \frac{10}{5} = 2 \text{ amp}$$

$$\therefore V_L = I X_L = 2 \times 15 = 30 \text{ V}$$

$$V_C = I X_C = 2 \times 11 = 22 \text{ V}$$

but V_L & V_C are in opposite phase \Rightarrow net voltage of L & C = $30 - 22 = 8$ volt

Q.29 [B]

Sol. $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

Q.30 [C]

Sol. $V_R = V_L = V_C = 10 \text{ V}$

$$\Rightarrow V_{\text{supply}} = 10 \text{ volt} \quad \& \quad R = X_L$$

After removing capacitor

$$V_{\text{supply}} = \sqrt{V_R^2 + V_L^2} \quad \therefore V_R = V_L$$

$$\Rightarrow V_L = \frac{10}{\sqrt{2}} \text{ volt}$$