


# MAHESH TUTORIALS SCIENCE

00 – 00		Q. Booklet Serial No: 120715	
Test No : 1211	3 Hrs.		Q. Booklet Version : 11


## Hints & Solutions

### PART A - PHYSICS

1. **b) From right to left**

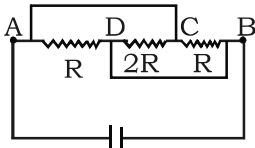

equivalent circuit is :

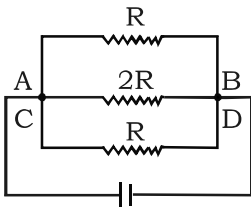

Right side of  $2R$  is at higher potential. so, Current will flow from right to left

2. **a) Zero**

In steady state both the capacitor will be fully charged and act as open circuit. Circuit is not complete, so, potential difference across all circuit element is zero.

3. **d) A will increase, V will decrease**



Initially  $R_v \rightarrow \infty$  If we add a resistance parallel to voltmeter

$$R_{\text{eff}} < R_v$$

$$I = \frac{V}{R} \text{ as } R \text{ decreases, } V \text{ will increase.}$$

Let the resistance of Ammeter is  $R_A$


Voltage across voltmeter is

$$V_r = \frac{V R_{\text{eff}}}{R_{\text{eff}} + R_A} = \frac{V}{1 + \frac{R_A}{R_{\text{eff}}}}$$

If  $R_{\text{eff}}$  decreases,  $V$  will also decrease.

4. **c)  $\frac{8}{7} \Omega$**

Circuit can be redrawn as :

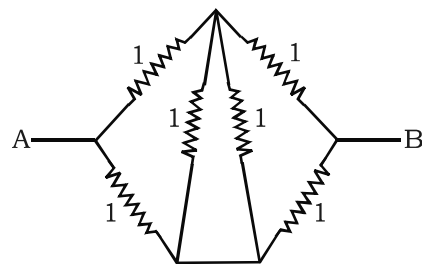

$$R_{\text{eq}} = \frac{8}{7} \Omega$$

5. **b)  $2C I^2 R^2$**

Current through the resistance parallel to capacitor is  $2I$

$$p.d = 2IR$$

So, potential difference across capacitor is  $2IR$ .

$$U = \frac{1}{2} CV^2 = \frac{1}{2} C(2IR)^2$$

$$= 2C I^2 R^2$$

6. **a) In all cases**

$$\text{Initially : } - \frac{R_1}{R_4} = \frac{R_2}{R_3}$$

If we change the position of cell and galvanometer. For zero deflection,

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\text{If } \frac{R_1}{R_4} = \frac{R_2}{R_3} \Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

i.e, if the bridge is balanced, by changing the position of galvanometer also it will be balanced.

7. **b) The potential difference between point X and ground would increase**

If switch is open, equivalent resistance of the circuit will increase. so, current will decrease. so, Pd between earth and x will increase.

8. **b)  $6.7 \times 10^{-4} \text{ Cm}^{-2}$**

$$dq = \sigma \cdot b \cdot dx$$

b is width

$$\frac{dq}{dt} = \sigma b \frac{dx}{dt}$$

$$I = \sigma b v$$

$$\sigma = \frac{I}{bV} = \frac{10^{-4}}{50\text{cm} \times 30\text{cm/s}}$$

$$\sigma = \frac{1}{15} \times 10^{-6}$$

$$\sigma = 6.7 \times 10^{-8} \text{ C cm}^{-2}$$

$$\sigma = 6.7 \times 10^{-4} \text{ C Cm}^{-2}$$

9. **c)  $\frac{\rho_1 + \rho_2}{2}$**

$$R = R_1 + R_2$$



$$\rho \frac{L_1 + L_2}{A} = \rho_1 \frac{L_1}{A} + \rho_2 \frac{L_2}{A}$$

$$\rho = \frac{\rho_1 L_1 + \rho_2 L_2}{L_1 + L_2}$$

If  $L_1 = L_2$

$$\rho = \frac{\rho_1 + \rho_2}{2}$$

10. **b)  $\frac{7r}{8}$**

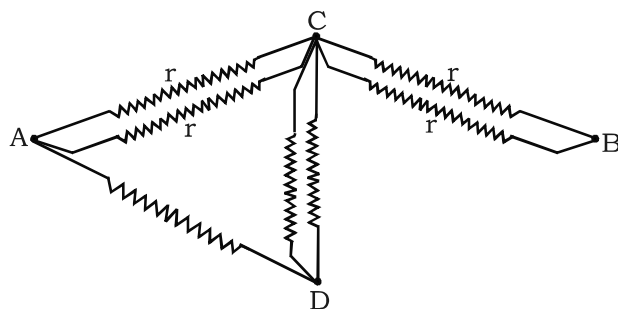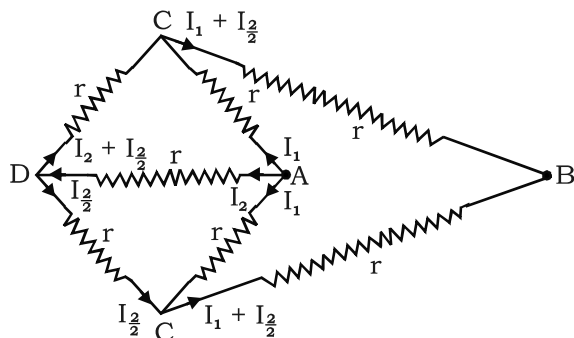

$$r_{eq} = \frac{\frac{3r}{2} \cdot \frac{r}{2}}{\frac{3r}{2} + \frac{r}{2}} + \frac{r}{2}$$

$$= \frac{3r}{8} + \frac{r}{2}$$

$$= \frac{7r}{8}$$

11. **a)  $20\Omega$**

Assume that we are connecting a resistance r.

so,

$$\frac{20}{20+r} = \frac{10}{5}$$

$$10 = \frac{20r}{20+r}$$

$$2r = 20 + r$$

$$r = 20\Omega$$

12. **a)  $\frac{2Rr}{R+r}$**

This is two balanced wheatstone bridge

$$\frac{1}{R_{eq}} = \frac{1}{4R} + \frac{1}{2r} + \frac{1}{4R}$$

$$\frac{1}{R_{eq}} = \frac{1}{2R} + \frac{1}{2r}$$

$$\frac{1}{R_{eq}} = \frac{(R+r)}{2Rr}$$

$$R_{eq} = \frac{2Rr}{R+r}$$

13. **b) D to B**

Without resistance R

$$V_D > V_B$$

So, Current will flow from D to B

14. **a) 300%**

Let initially resistance is r

Initial length is L and Area A.

As length increased by 100%, new length will be 2L. Let new Area is A'

V = const

$$LA = 2L \cdot A'$$

$$A' = \frac{A}{2}$$

$$\text{new resistance } r' = \rho \cdot \frac{2L}{\frac{A}{2}}$$

$$= 4r$$

$$\Delta r = 3r$$

$$\% \Delta r = \frac{\Delta r}{r} \times 100 = 300\%$$

15. **b)  $\frac{1}{3}$**

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$\frac{I_1}{I_2} = \frac{\frac{L_2}{A_2}}{\frac{L_1}{A_1}} = \frac{A_1}{A_2} \cdot \frac{L_2}{L_1}$$

$$= \frac{A_1 / A_2}{L_1 / L_2}$$

$$= \frac{\left(\frac{r_1}{r_2}\right)^2}{L_1 / L_2} \quad \frac{4/9}{4/3}$$

$$= \frac{1}{3}$$

16. **c)  $\frac{q\omega}{2\pi}$**

$$I = \frac{Q}{T} = \frac{q}{2\pi / \omega} = \frac{q\omega}{2\pi}$$

17. **a) is doubled**

$$V_d = \frac{eM}{me} E$$

If V is doubled, electric field will also be doubled. So,  $V_d$  is doubled.

18. **b) 700 K**

$$R = R_0 [1 + \alpha \Delta T]$$

$$1.5 = 1 [1 + 0.00125 \times (T - 300)]$$


$$0.5 = 0.00125(T - 300)$$

$$T - 300 = \frac{0.5000}{0.00125}$$

$$T - 300 = 400$$

$$T = 700 \text{ K}$$

19. **c) 7 ohm**

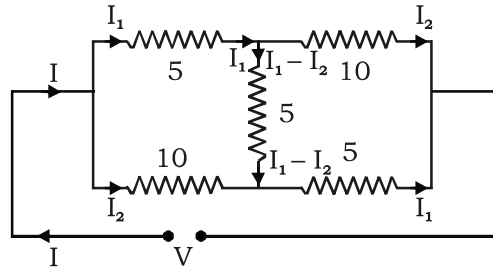

Let equivalent resistance is B

$$V = IR$$

$$I = I_1 + I_2 \quad \dots (i)$$

$$V = I_1 \cdot 5 + (I_1 - I_2) \cdot 5 + I_1 \cdot 5$$

$$V = 15 I_1 + 5 I_2 \quad \dots (ii)$$

$$V = I_1 \cdot 5 + I_2 \cdot 10 \quad \dots (iii)$$

from (ii) and (iii)

$$10 I_2 + 5 I_1 = V$$

$$15 I_1 - 5 I_2 = V \times 2$$

$$35 I_1 = 3V$$

$$I_1 = \frac{3V}{35}$$

$$10 I_2 + 5 I_1 = V$$

$$10 I_2 + \frac{15V}{35} = V$$

$$10 I_2 = V - \frac{15V}{35}$$

$$10 I_2 = \frac{20V}{35}$$

$$I_2 = \frac{2V}{35}$$

$$\begin{aligned} \therefore R &= \frac{V}{I} = \frac{V}{I_1 + I_2} \\ &= \frac{V}{\frac{3V}{35} + \frac{2V}{37}} = 7\Omega \end{aligned}$$

20. c) **9.85  $\Omega$**

4, 6, 12 and 20 are in parallel

$$\frac{1}{R_{1eq}} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} + \frac{1}{20}$$

$$\frac{1}{R_{1eq}} = \frac{15 + 10 + 5 + 3}{60}$$

$$= \frac{33}{60} = \frac{11}{20}$$

$$\frac{1}{R_{1eq}} = \frac{20}{11}$$

3, 5 and  $R_{1eq}$  are in series

$$R_{eq} = 8 + \frac{20}{11}$$

$$= \frac{108}{11} = 9.8$$

21. a) **1.7 A**

Junction rule,

$$I = 1.7 A$$

22. d)  $\frac{\alpha_1 + \alpha_2}{2}, \frac{\alpha_1 + \alpha_2}{2}$

$$R_1 = R_{o1} [1 + \alpha_1 \Delta T]$$

$$R_2 = R_{o2} [1 + \alpha_2 \Delta T]$$

For series

$$\begin{aligned} R &= R_1 + R_2 \\ &= R_{o1} [1 + \alpha_1 \Delta T] + R_{o2} [1 + \alpha_2 \Delta T] \end{aligned}$$

$$R_1 + R_2 = (R_{o1} + R_{o2}) + R_{o1} \alpha_1 \Delta T + R_{o2} \alpha_2 \Delta T$$

$$R_1 + R_2 =$$

$$(R_{o1} + R_{o2}) \left[ 1 + \frac{R_{o1} \alpha_1 \Delta T + R_{o2} \alpha_2 \Delta T}{R_{o1} + R_{o2}} \right]$$

$$R = R_0 \left[ 1 + \frac{R_{o1} \alpha_1 + R_{o2} \alpha_2}{R_{o1} + R_{o2}} \Delta T \right]$$

$$\alpha_{eff} = \frac{R_{o1} \alpha_1 + R_{o2} \alpha_2}{R_{o1} + R_{o2}}$$

If  $R_{o1} = R_{o2}$

$$\alpha_{eff} = \frac{\alpha_1 + \alpha_2}{2}$$

Similarly in case of parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{R_{o1} R_{o2}}{R_{o1} R_{o2}} (1 + \alpha \Delta T) =$$

$$\frac{R_{o1} (1 + \alpha_1 \Delta T) R_{o2} (1 + \alpha_2 \Delta T)}{R_{o1} (1 + \alpha_1 \Delta T) + R_{o2} (1 + \alpha_2 \Delta T)}$$

$$(1 + \alpha \Delta T) = \frac{(1 + \alpha_1 \Delta T)(1 + \alpha_2 \Delta T)}{\left( 1 + \frac{\alpha_1 + \alpha_2}{1} \Delta T \right)}$$

$$\begin{aligned} (1 + \alpha \Delta T) &= 1 + \left( \alpha_1 + \alpha_2 - \frac{\alpha_1 + \alpha_2}{2} \right) \Delta T \\ &= \alpha_1 + \alpha_2 \end{aligned}$$

23. b) **1.5 A**

$$R_{eq} = 2W$$

$$I = \frac{V}{R_{eq}} = \frac{3}{2} A$$

24. b) **Both have the same resistance**

$$A_s = 2A_R$$

$$L_s = 2L_R$$


$$\text{So, } \frac{L_s}{A_s} = \frac{L_R}{A_R}$$

$$I_s = I_R$$

25. b)  $\frac{E}{3R}$

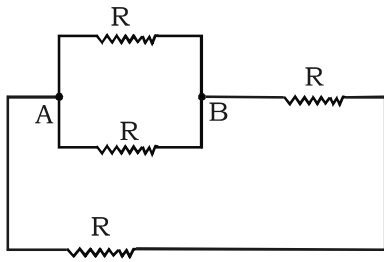26. c) **2 R/5**

The points which are earthed are connected



$$R_{eq} = \frac{\frac{R}{2} \cdot 2R}{\frac{R}{2} + 2R} = \frac{R^2}{5R/2} = 2R/5$$

27. d) **2.75 Ω**




Resistance of two parts will be

$$R_1 = \frac{\pi/6}{2\pi} R_0 = \frac{R_0}{12} = 3\Omega$$

$$R_2 = 33\Omega$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{33 \times 3}{36} = \frac{33}{12} \Omega = 2.75 \Omega$$

28. a) **20 volt**

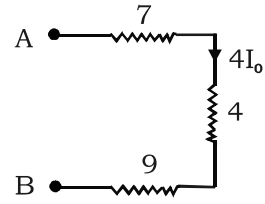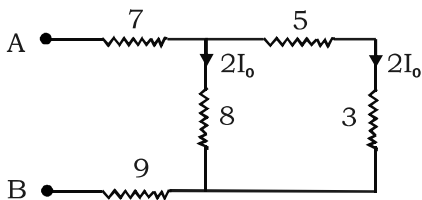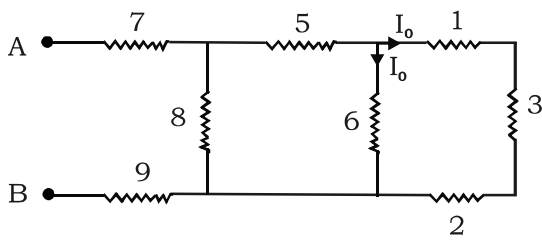

$$V = 20.4 I_0$$

$$V = 80 \cdot 0.25$$

$$V = 80 \times \frac{25}{100}$$


$$V = 20V$$

29. a) **4 rows, 6 cells in a row**

$$\frac{r}{R} = \frac{m}{n}$$

$$m = 4, \quad n = 6$$

30. c) **12 volt**

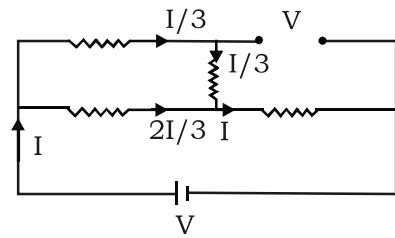

$$V = 15V$$

$$R_{eq} = 5R/3 = 5W$$










$$I = 3A$$

$$V = \frac{1}{3}R + I R$$

$$V = \frac{3}{3} \cdot 3 + 3 \cdot 3$$

$$V = 12V$$

## PART B - CHEMISTRY

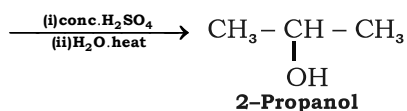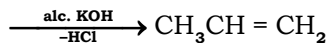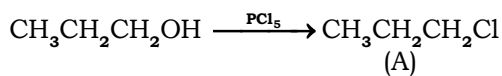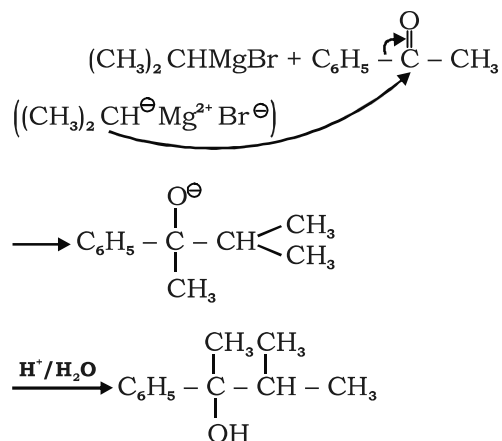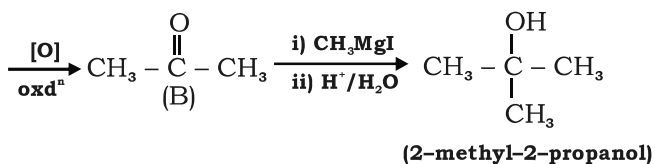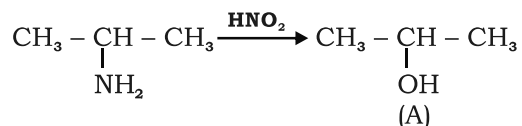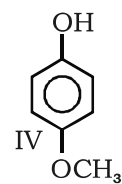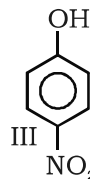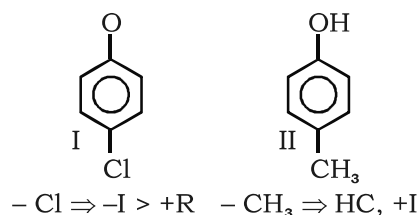31. c) **2-propanol**32. c) **(CH<sub>3</sub>)<sub>2</sub>CHMgBr acid hydrolysis**33. d) **2-methyl-2-propanol**34. d) **III > I > II > IV**

EWG increases acidic strength.  
III > I > II, IV

35. b) **CH<sub>3</sub>OH**




rate of esterification ∝

$$\frac{1}{\text{steric hindrance on alkyl group of alcohol as well as acid}}$$
36. c) **Acetylene**


only 1 π bond can be formed  
∴ acetylene can't be formed






37. c) **Tertiary alcohol by S<sub>N</sub>1**Lucas test follows S<sub>N</sub>1 mechanism

38. c)


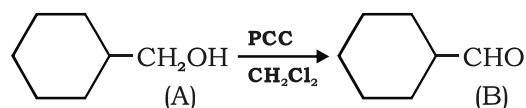
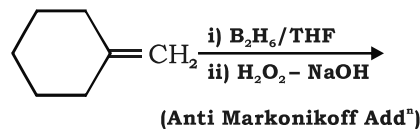
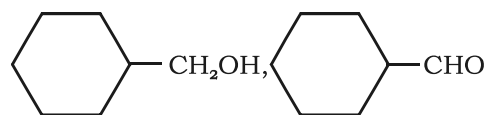
39. c) **isobutyl alcohol**

+ve Iodoform test can be shown by.


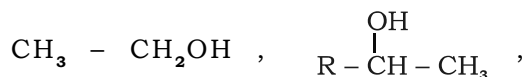


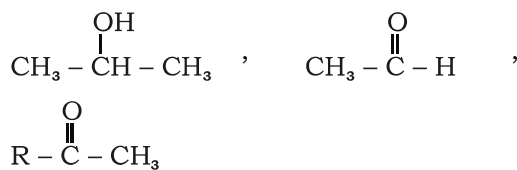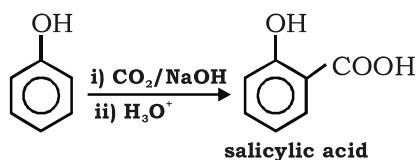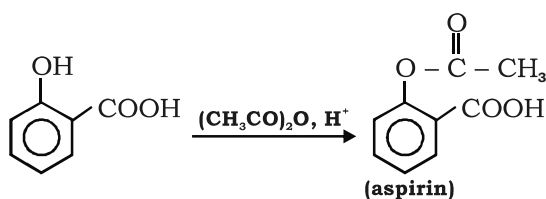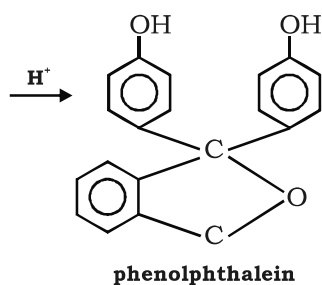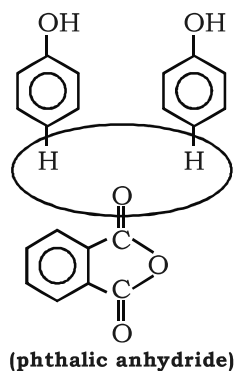40. b) **salicylic acid**41. b)  **$(\text{CH}_3\text{CO})_2\text{O}, \text{H}^+$** 42. a) **phenolphthalein**


43. c)

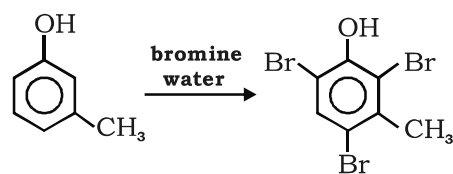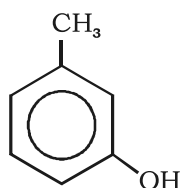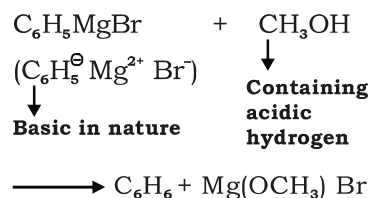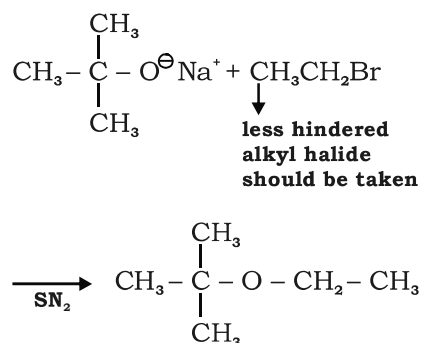44. a)  **$\text{C}_6\text{H}_6$** 45. c) **sodium tert-butoxide and ethyl bromide**Williamson's synthesis follows  $\text{S}_{\text{N}}2$  reaction46. a)  **$\text{CHCl}_3/\text{NaOH}$** 


Reimer-Tiemann Reaction

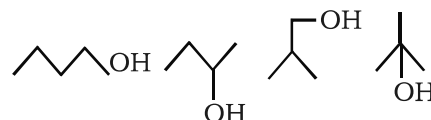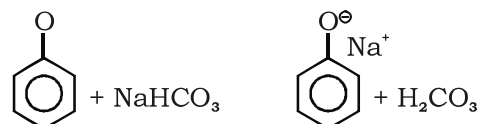47. d) **Neutral  $\text{FeCl}_3$**  $\text{FeCl}_3$  is used to test enol form48. d) **4**49. a) **sodium bicarbonate**


$\text{H}_2\text{CO}_3$  is stronger acid than phenol  
Rule : Strong acid displace weak acid

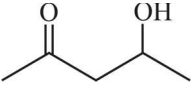
50. a)   
Formation of conjugated system which is stabilised due to resonance. Also  $\beta$ -Hydrogen is acidic in option (a)


51. c) **salicylic acid**

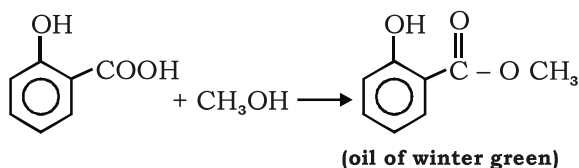






52. d) **2, 4, 6-tribromophenol**

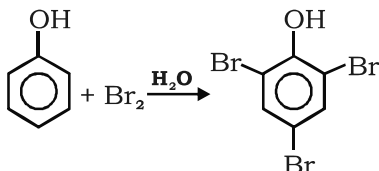

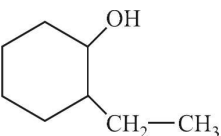53. d) 

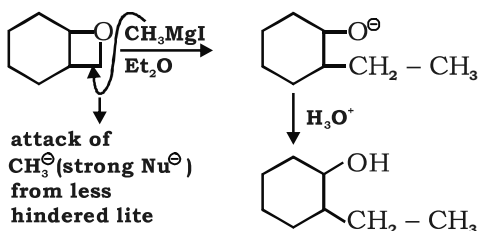

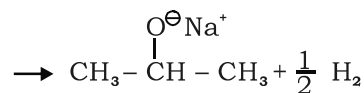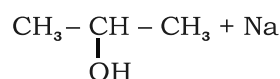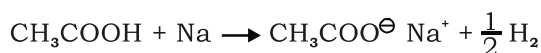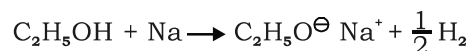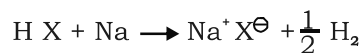54. b)  **$\text{CH}_3-\text{O}-\text{CH}_3$**   
Na reacts with compound having acidic hydrogen and releases  $\text{H}_2$  gas.



$\text{CH}_3-\text{O}-\text{CH}_3 + \text{Na}$   
(doesn't contain acidic Hydrogen)  
Acidic Hydrogen or active Hydrogen means Hydrogen attached to more electronegative atom.

55. a) **in presence of  $\text{H}_2\text{SO}_4$  at 413 K**  
Ether is formed lower temp (413 K)  
Alkene is formed at relatively higher temp (443 K)

56. d) **a sulphide ore**  
sulphide ores separated by froth floatating method which is based on different wettability

57. b) **silver**  
Fact

58. b) **a reducing agent**  
Al is used to reduce the other metal.

59. d) **All**  
Copper glance  $\rightarrow \text{Cu}_2\text{S}$   
Galena  $\rightarrow \text{PbS}$   
Iron pyrites  $\rightarrow \text{FeS}_2$  } Roasting is required for sulphide ores to convert into oxides

60. c) **slagging**  
Fact